

Chapter 7, Problem 38.

A circuit is described by

$$\frac{di}{dt} + 3i = 2u(t),$$

find $i(t)$ for $t > 0$ given that $i(0) = 0$.