

Chapter 5, Problem 4

The output voltage of an op amp is .4 V when the noninverting input is 1 mV. If the open-loop gain of the op amp is 2×10^6 , what is the inverting input?