

Chapter 10, Problem 94.

Design a Colpitts oscillator that will operate at 50 kHz.