

### Chapter 7, Solution 23.

Since the  $2\ \Omega$  resistor,  $1/3\ \text{H}$  inductor, and the  $(3+1)\ \Omega$  resistor are in parallel, they always have the same voltage.

$$-i = \frac{10}{2} + \frac{10}{3+1} = 7.5 \longrightarrow i(0) = -7.5$$

The Thevenin resistance  $R_{\text{th}}$  at the inductor's terminals is

$$R_{\text{th}} = 2 \parallel (3+1) = \frac{4}{3}, \quad \tau = \frac{L}{R_{\text{th}}} = \frac{1/3}{4/3} = \frac{1}{4}$$

$$i(t) = i(0)e^{-t/\tau} = -7.5e^{-4t}, \quad t > 0$$

$$v_L = v_o = L \frac{di}{dt} = -7.5(-4)(1/3)e^{-4t}$$

$$v_o = 10e^{-4t}\ \text{V}, \quad t > 0$$

$$v_x = \frac{1}{3+1}v_L = 2.5e^{-4t}\ \text{V}, \quad t > 0$$