

Chapter 7, Problem 3.

Determine the time constant for the circuit in Fig. 7.83

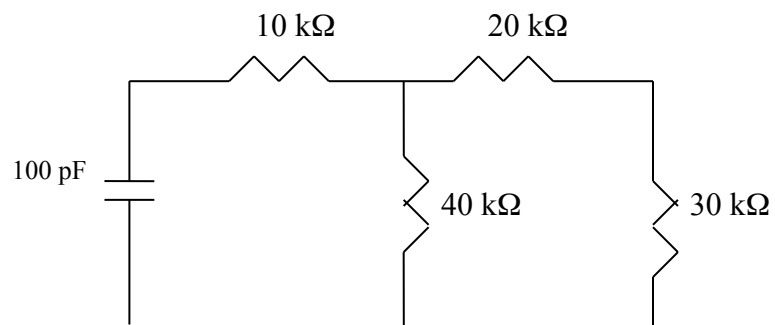


Figure 7.83
For Prob. 7.3.