

Chapter 10, Problem 81.

Use PSpice to determine V_o in the circuit of Fig. 10.124. Assume $\omega=1$ rad/s

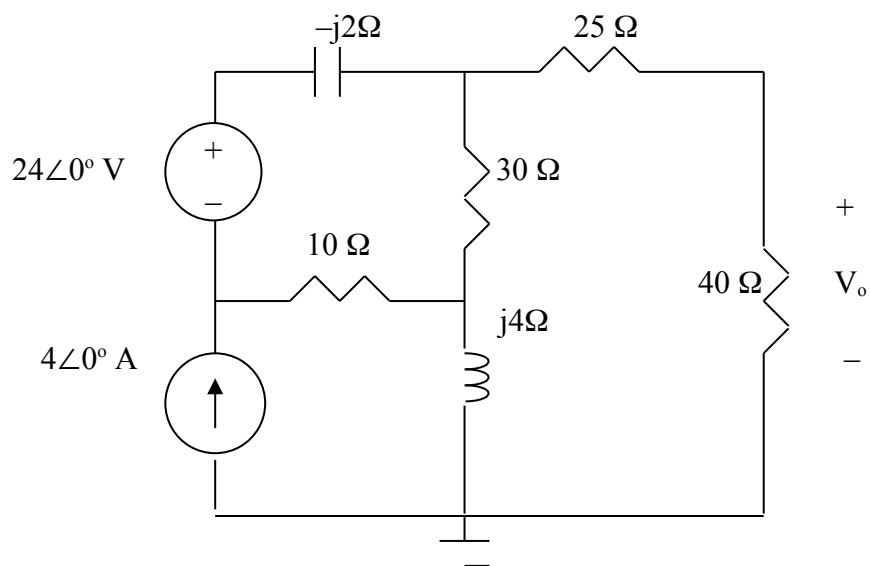


Figure 10.124
For Prob. 10.81.