

Chapter 6, Solution 43.

The current in an 80-mH inductor increases from 0 to 60 mA. How much energy is stored in the inductor?

Solution

$$\begin{aligned}w &= L \int_{-\infty}^t i dt = \frac{1}{2} Li^2(t) - \frac{1}{2} Li^2(-\infty) \\&= \frac{1}{2} \times 80 \times 10^{-3} \times (60 \times 10^{-3})^2 - 0 \\&= 144 \mu\text{J}.\end{aligned}$$