

### Chapter 5, Solution 77.

The schematic for the PSpice solution is shown below.

Note that the output voltage,  $-6.686\text{ mV}$ , agrees with the answer to problem, 5.48.

