

**Chapter 10, Problem 40.**

Find  $i_o$  in the circuit shown in Fig. 10.85 using superposition.

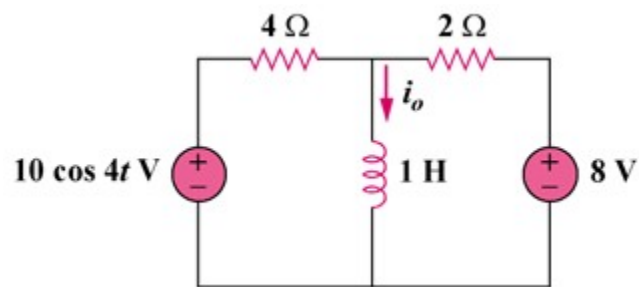


Figure 10.85  
For Prob. 10.40.