

**Chapter 7, Problem 63.**

Obtain  $v(t)$  and  $i(t)$  in the circuit of Fig. 7.128.

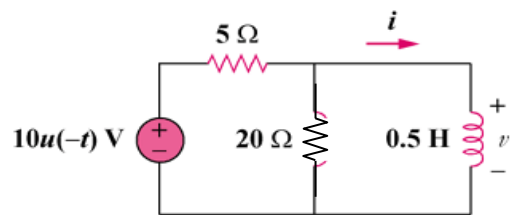


Figure 7.128  
For Prob. 7.63.