

Chapter 9, Solution 54.

In the circuit of Fig. 9.61, find V_s if $I_o = 2\angle 0^\circ$ A.


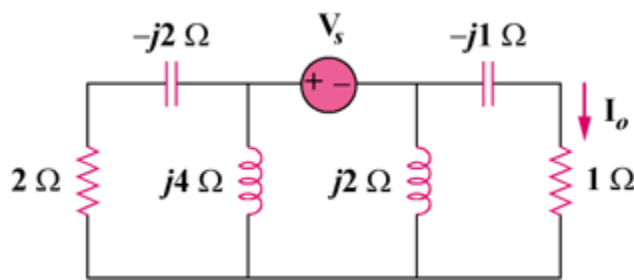


Figure 9.61
For Prob. 9.54.

Solution

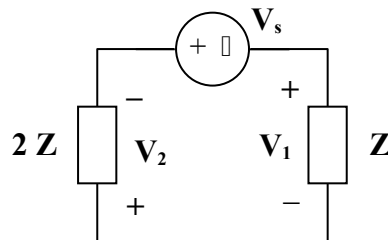Since the left portion of the circuit is twice as large as the right portion, the equivalent circuit is shown below.



$$V_1 = I_o(1 - j) = 2(1 - j)$$

$$V_2 = 2V_1 = 4(1 - j)$$

$$V_2 + V_s + V_1 = 0 \text{ or}$$

$$V_s = -V_1 - V_2 = -6(1 - j) = (6\angle 180^\circ)(1.4142\angle -45^\circ)$$

$$V_s = 8.485\angle 135^\circ \text{ V}$$