

**Chapter 9, Problem 53.**

Find  $\mathbf{I}_\theta$  in the circuit in Fig. 9.60.

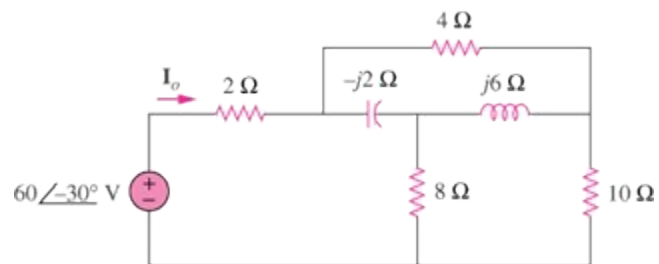


Figure 9.60  
For Prob. 9.53.