

**Chapter 7, Problem 43.**

Consider the circuit in Fig. 7.110. Find  $i(t)$  for  $t < 0$  and  $t > 0$ .

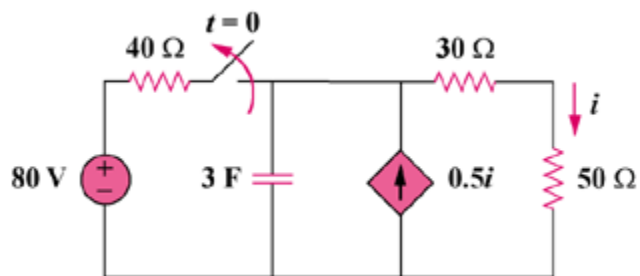


Figure 7.110  
For Prob. 7.43.