

Chapter 11, Problem 63.

Find \mathbf{I}_o in the circuit of Fig. 11.82.

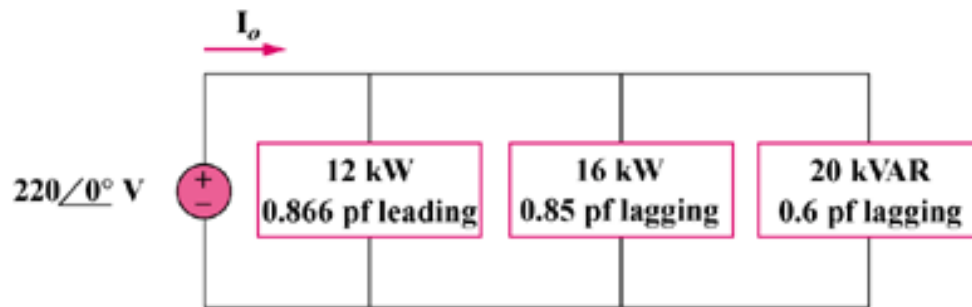


Figure 11.82

For Prob. 11.63.