
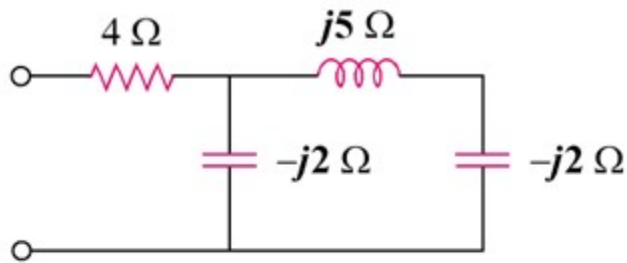


Chapter 11, Problem 41.

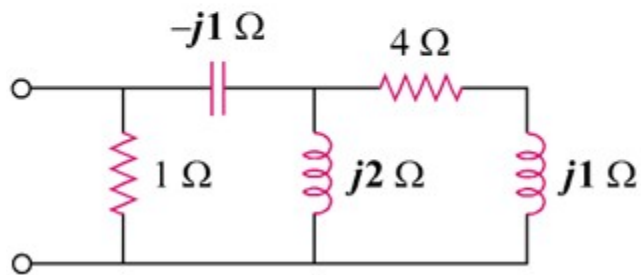Obtain the power factor for each of the circuits in Fig. 11.68. Specify each power factor as leading or lagging.



(a)



(b)

Figure 11.68
For Prob. 11.41.