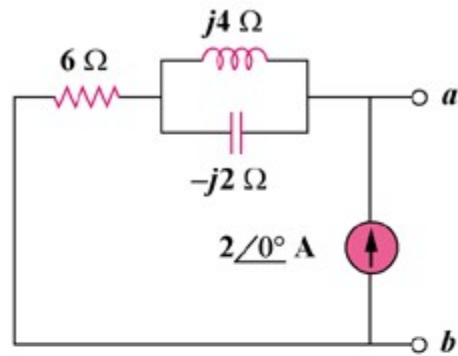
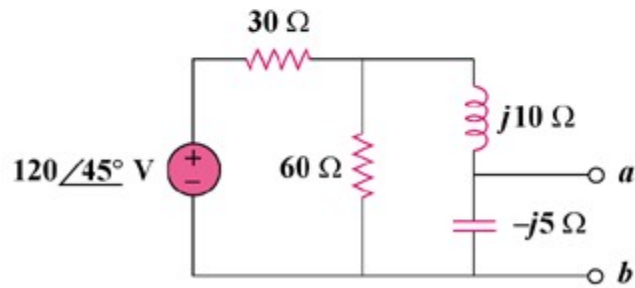


### Chapter 10, Problem 56.

For each of the circuits in Fig. 10.99, obtain Thevenin and Norton equivalent circuits at terminals  $a$ - $b$ .



(a)



(b)

Figure 10.99  
For Prob. 10.56.