

Chapter 9, Problem 75.

Design a circuit that will transform a sinusoidal input to a cosinusoidal output.