

Chapter 7, Problem 59.

Determine the step response $v_o(t)$ to $v_s = 18 u(t)$ V in the circuit of Fig. 7.124.

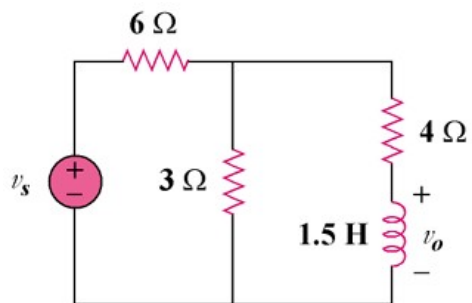


Figure 7.124
For Prob. 7.59.