

Chapter 10, Problem 37.

Use mesh analysis to find currents \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{I}_3 in the circuit in Fig. 10.82

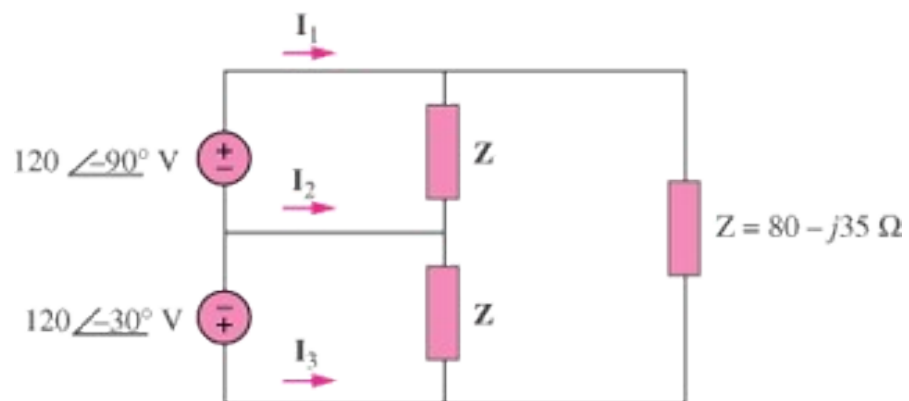


Figure 10.82
For Prob. 10.37.