

**Chapter 7, Problem 33.**

The voltage across a 10-mH inductor is  $45\delta(t - 2)$  mV. Find the inductor current, assuming that the inductor is initially uncharged.