

Chapter 10, Problem 61.

Find the Thevenin equivalent at terminals a-b of the circuit in Fig. 10.104.

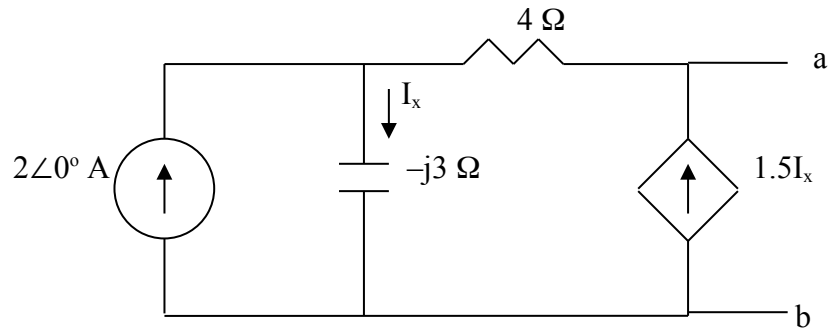


Figure 10.104
For Prob. 10.61.