

**Chapter 6, Problem 79.**

Design an analog computer circuit to solve the following ordinary differential equation.

$$(dy(t)/dt) + 4y(t) = f(t)$$

where  $y(0) = 1$  V.