

Chapter 9, Problem 28.

Determine the current that flows through a $15\text{-}\Omega$ resistor connected in parallel with a voltage source $v_s = 156 \cos(377t + 45^\circ)$ V.