

**Chapter 5, Problem 59.**

In the op amp circuit of Fig. 5.86, determine the voltage gain  $v_o/v_s$ . Take  $R = 10\text{ k}\Omega$ .

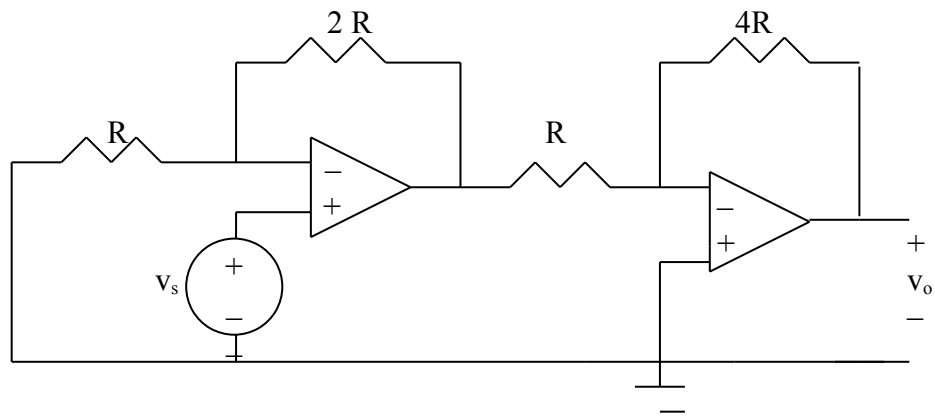


Figure 5.86  
For Prob. 5.59.