

**Chapter 7, Problem 21.**

In the circuit in Fig. 7.101, find the value of  $R$  for which the steady-state energy stored in the inductor will be 1 J.

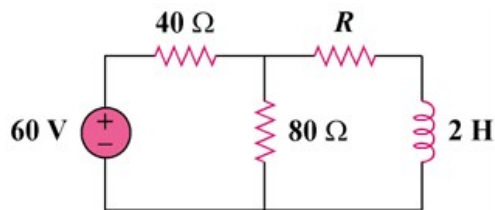


Figure 7.101  
For Prob. 7.21.