

**Chapter 11, Problem 88.**

A certain electronic circuit is connected to a 110-V ac line. The root-mean-square value of the current drawn is 2 A, with a phase angle of  $55^\circ$ .

- (a) Find the true power drawn by the circuit.
- (b) Calculate the apparent power.