

**Chapter 10, Problem 48.**

Find  $i_o$  in the circuit in Fig. 10.93 using superposition.

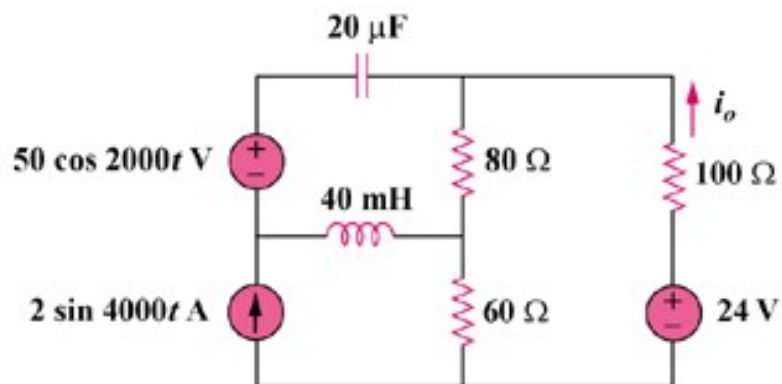


Figure 10.93  
For Prob. 10.48.