

**Chapter 10, Problem 16.**

Use nodal analysis to find  $V_x$  in the circuit shown in Fig. 10.65.

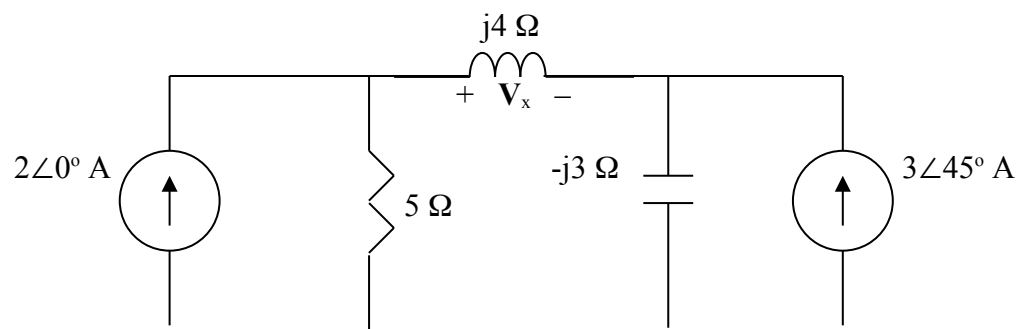


Figure 10.65  
For Prob. 10.16.