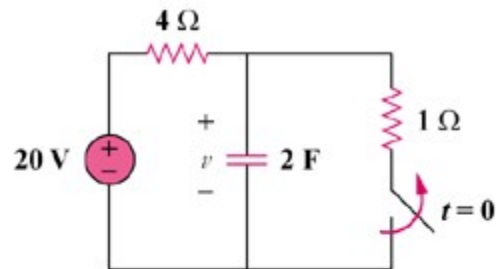
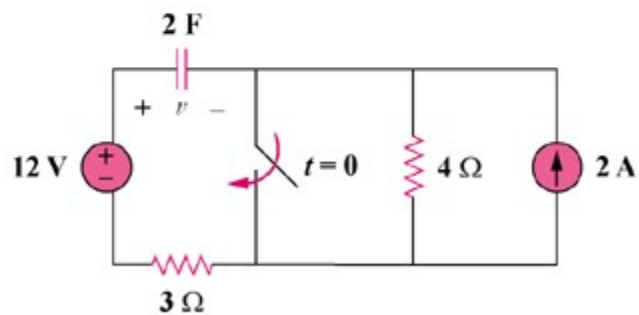


**Chapter 7, Problem 39.**

Calculate the capacitor voltage for  $t < 0$  and  $t > 0$  for each of the circuits in Fig. 7.106.



**(a)**



**(b)**

Figure 7.106  
For Prob. 7.39.