

## Chapter 11, Solution 91

The nameplate of an electric motor has the following information:

Line voltage: 220 V rms

Line current: 15 A rms

Line frequency: 60 Hz

Power: 2700 W

Determine the power factor (lagging) of the motor. Find the value of the capacitance  $C$  that must be connected across the motor to raise the pf to unity.

### Solution

$I = V/Z$  which leads to  $Z = [220/15] \angle \theta = 14.6667 \angle \theta$ ,  $S = (220)(15) \angle \theta = 3.3 \angle \theta$  kVA, where  $\cos^{-1}(2700/3300) = \cos^{-1}(0.818182) = 35.097^\circ$ , and  $X_L = 3300 \sin(35.097^\circ) = 1897.38 = X_C$ . This leads to  $C = 1/[377(1897.38)] = \mathbf{1.398 \mu F}$ .

$$\text{pf} = \mathbf{0.8182 \text{ (lagging)}}$$

$$C = \mathbf{1.398 \mu F}$$

$$\mathbf{0.8182 \text{ (lagging)}, 1.398 \mu F}$$