

Chapter 7, Problem 89.

An RL circuit may be used as a differentiator if the output is taken across the inductor and $t \ll T$ (say $t < 0.1 T$), where T is the width of the input pulse. If R is fixed at $200 \text{ k}\Omega$, determine the maximum value of L required to differentiate a pulse with $T = 10 \text{ }\mu\text{s}$.