

### Chapter 11, Solution 67.

For the op amp shown in Fig. 11.86, calculate:

- the complex power delivered by the voltage source
- the average power dissipated by the  $12\text{-}\Omega$  resistor

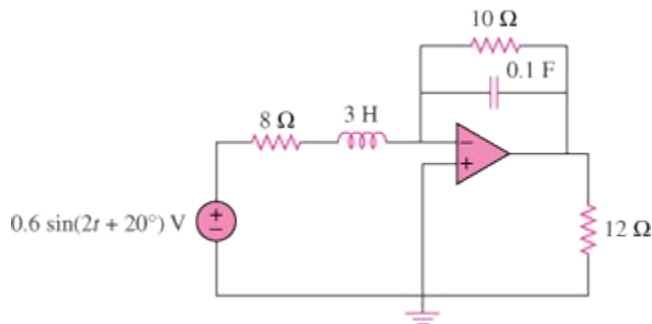



Figure 11.86  
For Prob. 11.67.

### Solution

$$\omega = 2, \quad 3\text{ H} \longrightarrow j\omega L = j6, \quad 0.1\text{ F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j2 \times 0.1} = -j5$$

$$10 \parallel (-j5) = \frac{-j50}{10 - j5} = 2 - j4$$

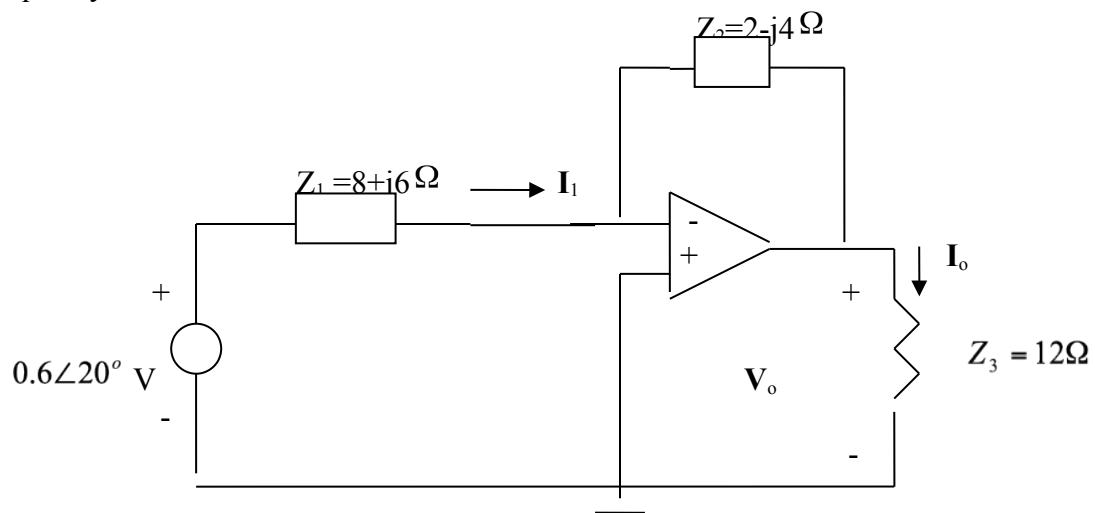The frequency-domain version of the circuit is shown below.



$$(a) \quad I_1 = \frac{0.6 \angle 20^\circ - 0}{8 + j6} = \frac{0.5638 + j0.2052}{8 + j6} = 0.06 \angle -16.87^\circ$$

$$S = \frac{1}{2} V_s I_1^* = (0.3 \angle 20^\circ)(0.06 \angle +16.87^\circ) = \underline{14.4 + j10.8 \text{ mVA}} = \underline{18 \angle 36.86^\circ \text{ mVA}}$$

$$\mathbf{S = (14.4+j10.8) mVA = 18 \angle 36.86^\circ mVA}$$

$$(b) \quad V_o = -\frac{Z_2}{Z_1} V_s, \quad I_o = \frac{V_o}{Z_3} = -\frac{(2-j4)}{12(8+j6)} (0.6 \angle 20^\circ) = 0.0224 \angle 99.7^\circ$$

$$P = \frac{1}{2} |I_o|^2 R = 0.5(0.0224)^2 (12) = \underline{2.904 \text{ mW}}$$

$$\mathbf{P = 2.904 \text{ mW}}$$

**(a)  $18 \angle 36.86^\circ \text{ mVA}$ , (b)  $2.904 \text{ mW}$**