

**Chapter 7, Solution 84.**

The resistance of a 160-mH coil is  $8\Omega$ . Find the time required for the current to build up to 60% of its final value when voltage is applied to the coil.

**Solution**

Let  $I_o$  be the final value of the current. Then

$$i(t) = I_o(1 - e^{-t/\tau}), \quad \tau = R/L = 0.16/8 = 1/50$$

$$0.6I_o = I_o(1 - e^{-50t}) \quad \longrightarrow \quad t = \frac{1}{50} \ln \frac{1}{0.4} = \underline{18.33 \text{ ms.}}$$