

**Chapter 6, Problem 28.**

Obtain the equivalent capacitance of the network shown in Fig. 6.58.

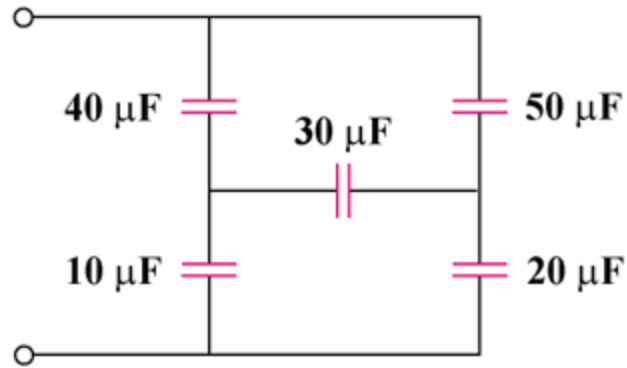


Figure 6.58  
For Prob. 6.28.