

Chapter 10, Problem 47.

Determine i_o in the circuit of Fig. 10.92 using the superposition principle.

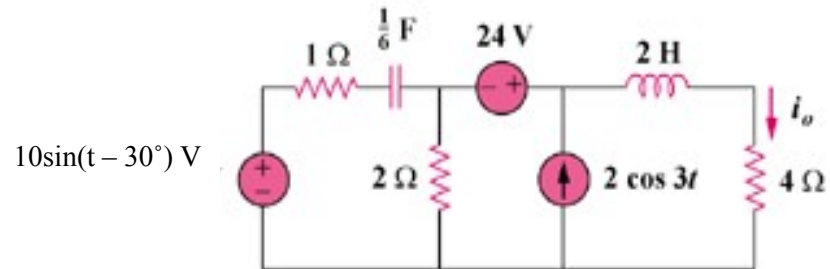


Figure 10.92
For Prob. 10.47.