## Chapter 9, Solution 20.

 $7.5\cos(10t+30^\circ)$  A can be represented by  $7.5\angle30^\circ$  and  $120\cos(10t+75^\circ)$  V can be represented by  $120\angle75^\circ$ . Thus,

$$Z = V/I = (120 \angle 75^{\circ})/(7.5 \angle 30^{\circ}) = 16 \angle 45^{\circ}$$
 or (11.314+j11.314) Ω.