


### Chapter 5, Solution 8.

- (a) If  $v_a$  and  $v_b$  are the voltages at the inverting and noninverting terminals of the op amp.


$$v_a = v_b = 0$$

$$1\text{mA} = \frac{0 - v_o}{2\text{k}} \longrightarrow v_o = -2\text{ V}$$

- (b)

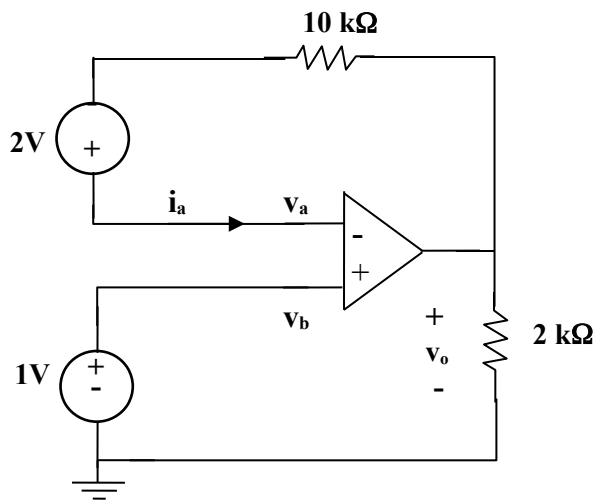

(a)

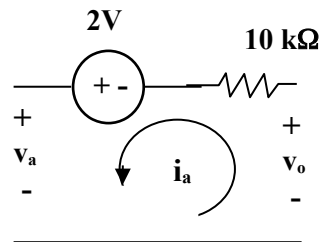

(b)

Since  $v_a = v_b = 1\text{V}$  and  $i_a = 0$ , no current flows through the 10kΩ resistor. From Fig. (b),

$$-v_a + 2 + v_o = 0 \longrightarrow v_o = v_a - 2 = 1 - 2 = -1\text{V}$$