

Chapter 5, Problem 91

A noninverting current amplifier is portrayed in Fig. 5.108. Calculate the gain i_o/i_s . Take $R_1 = 8\text{ k}\Omega$ and $R_2 = 1\text{ k}\Omega$.

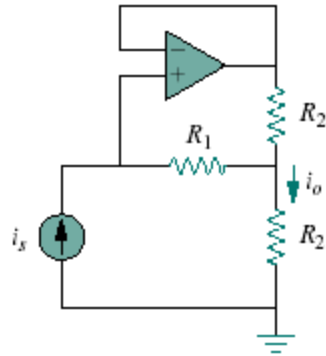


Figure 5.108
For Prob. 5.91.