

Chapter 10, Problem 4.

Compute $v_o(t)$ in the circuit of Fig. 10.53.

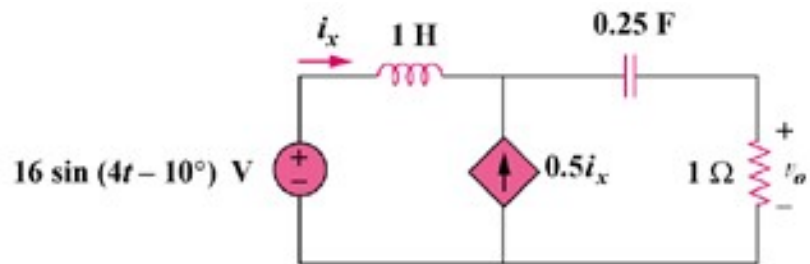


Figure 10.53
For Prob. 10.4.