Chapter 10, Problem 6.

Determine V_x shown in Fig. 10.55

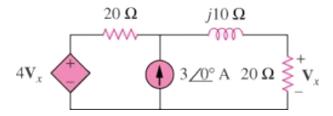


Figure 10.55 For Prob. 10.6.