

**Chapter 7, Problem 69.**

For the op amp circuit in Fig. 7.134, find  $v_o(t)$  for  $t > 0$ .

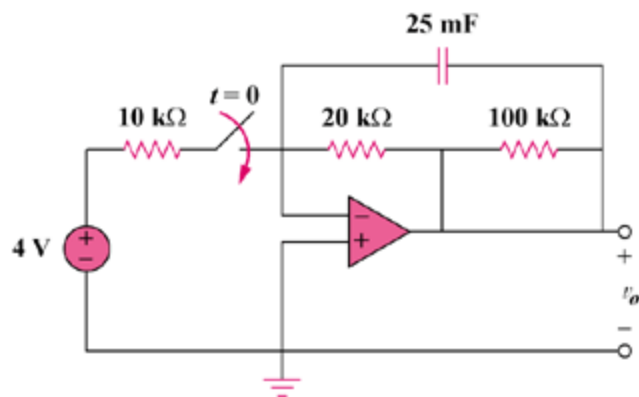


Figure 7.134  
For Prob. 7.69.