

Chapter 11, Problem 7.

Given the circuit of Fig. 11.40, find the average power absorbed by the $10\text{-}\Omega$ resistor.

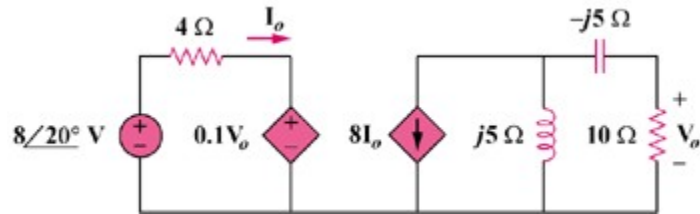


Figure 11.40
For Prob. 11.7.