

Chapter 10, Problem 7.

Use nodal analysis to find \mathbf{V} in the circuit of Fig. 10.56

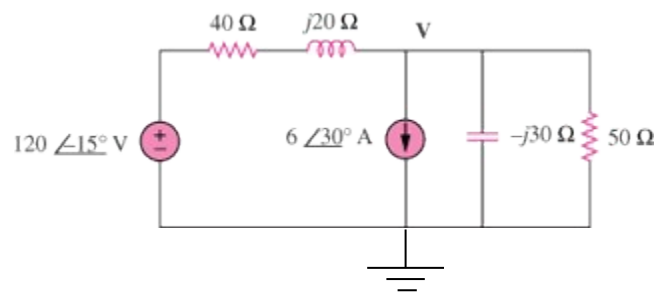


Figure 10.56
For Prob. 10.7.