

**Chapter 10, Problem 51.**

Using the circuit in Prob. 10.42, design a problem to help other students to better understand source transformation.