

Chapter 9, Problem 34.

What value of ω will cause the forced response, v_o , in Fig. 9.41 to be zero?

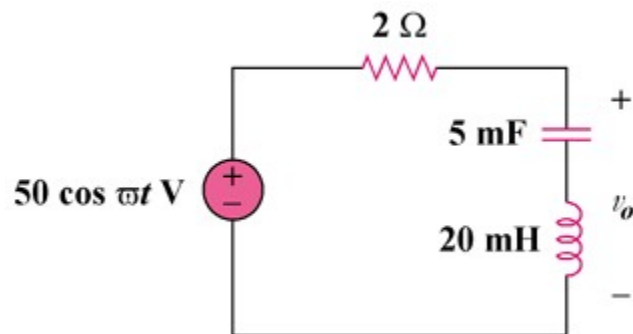


Figure 9.41
For Prob. 9.34.