

Chapter 10, Problem 36.

Compute V_o in the circuit of Fig. 10.81 using mesh analysis.

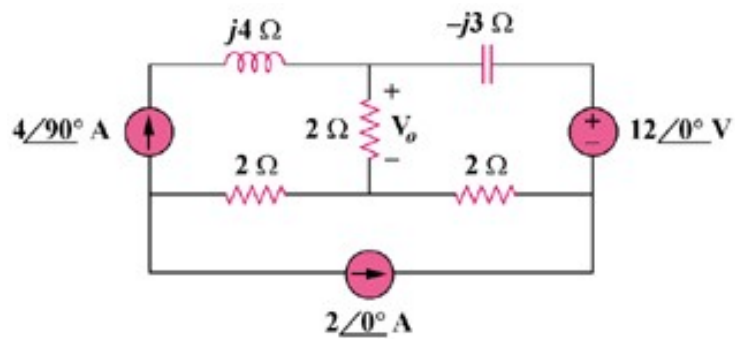


Figure 10.81
For Prob. 10.36.