

### Chapter 10, Solution 59.

Calculate the output impedance of the circuit shown in Fig. 10.102.


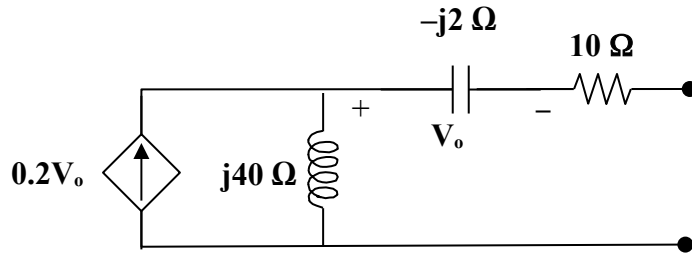


Figure 10.102  
For Prob. 10.59.
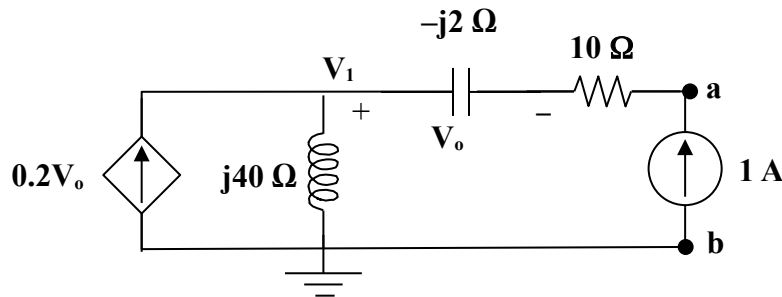
### Solution

Since there are no independent sources, we need to inject a current, best value is to make it 1 amp, into the terminals on the right and then to determine the voltage at the terminals.



Clearly  $V_o = -(-j2) = j2$  and  $V_1 = (0.2V_o + 1)j40 = (1 + j0.4)j40 = -16 + j40$  V.  
Next,  $V_{ab} = 10 - j2 - 16 + j40 = -6 + j38 = 38.47 \angle 98.97^\circ$  V or

$$Z_{eq} = (-6 + j38) \Omega.$$