

**Chapter 9, Problem 60.**

Obtain  $\mathbf{Z_{in}}$  for the circuit shown in Fig. 9.67.

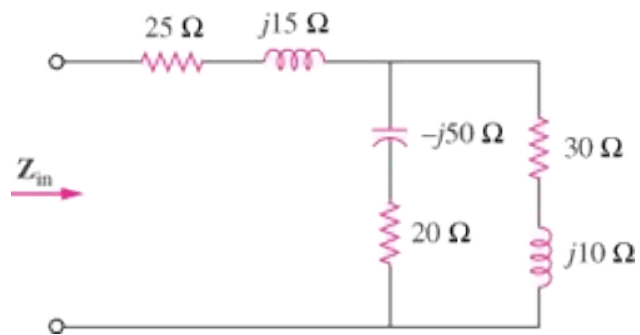


Figure 9.67  
For Prob. 9.60.