

Chapter 7, Problem 6.

The switch in Fig. 7.85 has been closed for a long time, and it opens at $t = 0$. Find $v(t)$ for $t \geq 0$.

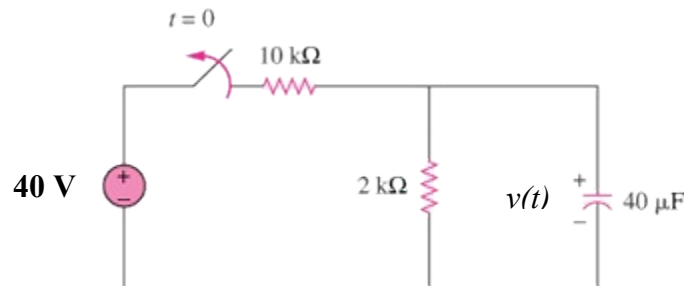


Figure 7.85
For Prob. 7.6.