

**Chapter 11, Problem 42.**

A 110-V rms, 60-Hz source is applied to a load impedance  $Z$ . The apparent power entering the load is 120 VA at a power factor of 0.707 lagging.

- (a) Calculate the complex power.
- (b) Find the rms current supplied to the load.
- (c) Determine  $Z$ .
- (d) Assuming that  $Z = R + j\omega L$ , find the values of  $R$  and  $L$ .